

Practical – 05

Class: - B.E.E&TC

Subject: - VLSI Design and Technology

Aim: - To implement an inverter (not gate), NAND, NOR gate & 1 Bit Half Adder using CMOS technology

Theory :-

A] CMOS Inverter:


A logic inverter can be constructed by using one P-MOS and N-MOS inverter when there is '0' at input, then output is '1' and vice versa. In general a fully complementary always has an n-switch in pull down at output.

Truth table of Inverter:-

| INPUT | OUTPUT |
|-------|--------|
| 0 | 1 |
| 1 | 0 |

This is truth table of logic inverter where when there is a '0' at the input the output is '1' and when there is '1' at the input one output will zero.

Schematic of CMOS Inverter

 


B) CMOS NAND Gate

Theory :- NAND Gate is formed by connecting an inverter i.e. NOT gate at the output of an AND gate

Truth Table:-

| Input | | Outputs |
|-------|---|---------|
| A | B | C |
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Schematic of CMOS NAND Gate:

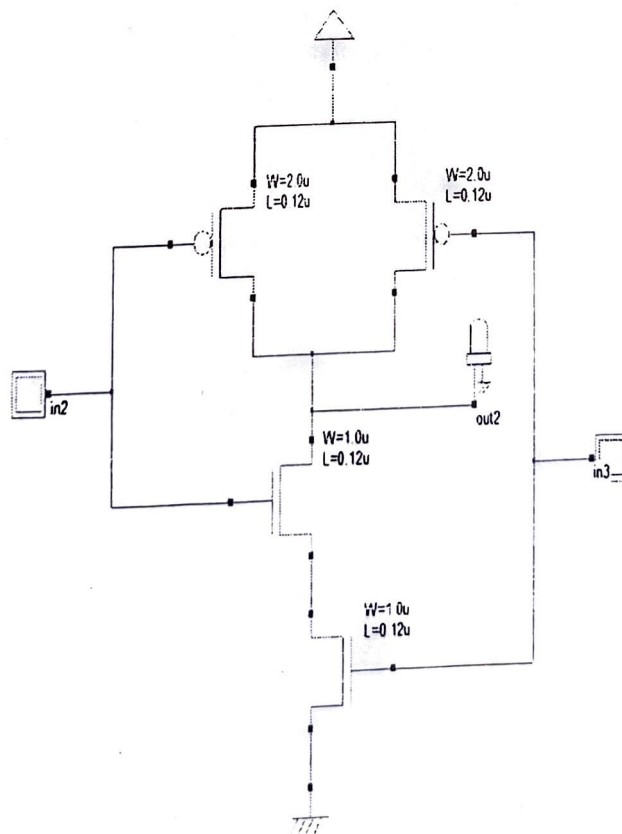

NAME OF THE STUDENT:

CLASS:

ROLL NO:

Observation Table:

- **Effect of Capacitor on Power Dissipation**

| Sr No | Capacitor | Power Dissipation |
|-------|----------------------------|-------------------|
| 1 | Without Capacitor | 5.909 μW |
| 2 | With Capacitor (0.01pF) | 17.908 μW |

Conclusion: -

In this experiment we implement NAND gate using CMOS inverter


C| CMOS NOR Gate:

Theory :- A 2 input NOR gate can be constructed using NMOS & PMOS .

Truth Table:-

| Input | | Outputs |
|-------|---|---------|
| A | B | C |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Schematic of CMOS NOR Gate:

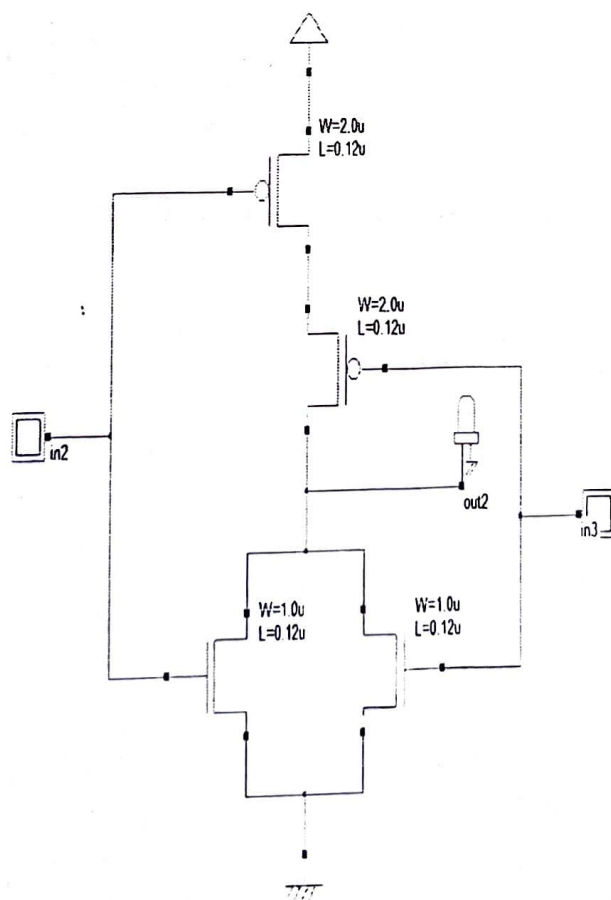

Observation Table:

- **Effect of Capacitor on Power Dissipation**

| Sr No | Capacitor | Power Dissipation |
|-------|----------------------------|-------------------|
| 1 | Without Capacitor | 5.028 μ W |
| 2 | With Capacitor (0.01pF) | 12.295 μ W |

Conclusion: - In this experiment we implement NOR gate using capacitor and without capacitor

NAME OF THE STUDENT:
CLASS:
ROLL NUMBER:

Practical - 06

Class: - B.E.E&TC


Subject: - VLSI Design and Technology

Aim: - To design and implement CMOS 2:1 multiplexer using Transmission gate & also comment on no. of pass transistors required to implement the same.


Theory: -

Transmission Gates

 
- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

 

$g = 1, gb = 0$

 

Input




Output

$g = 1, gb = 0$

$0 \rightarrow \text{strong } 0$

$g = 1, gb = 0$


$1 \rightarrow \text{strong } 1$

   

Multiplexers Using Transmission Gate

- 2:1 *multiplexer* chooses between two inputs

| S | D1 | D0 | Y |
|---|----|----|---|
| 0 | X | 0 | 0 |
| 0 | X | 1 | 1 |
| 1 | 0 | X | 0 |

 

NAME OF THE STUDENT:

CLASS:

ROLL NUMBER:

Practical - 07

Class: - B.E.E&TC

Subject: - VLSI Design and Technology


Aim: Design of CMOS single bit SRAM cell layout and verify the functionality by simulation

Procedure:

Prepare the CMOS layout of single bit SRAM cell. Do the functional simulation and verify the results.

Comment on the effect of no load and capacitive load on rise time and fall time.

Circuit Diagram:

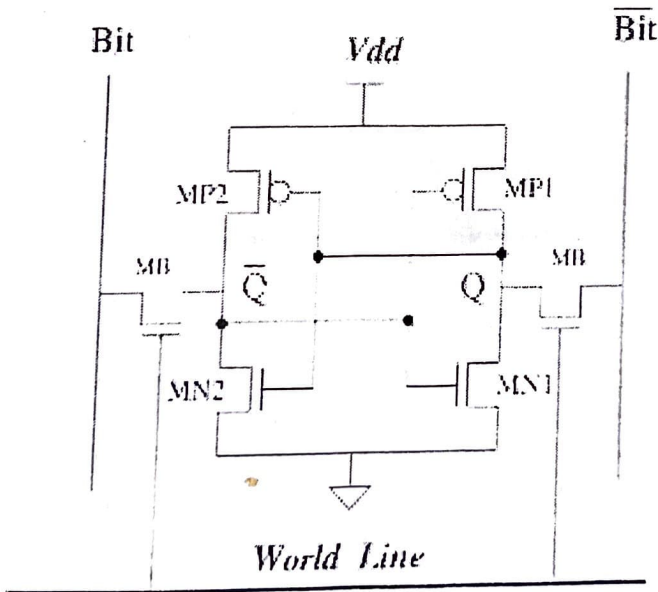

NAME OF THE STUDENT:
CLASS:
ROLL NUMBER: